
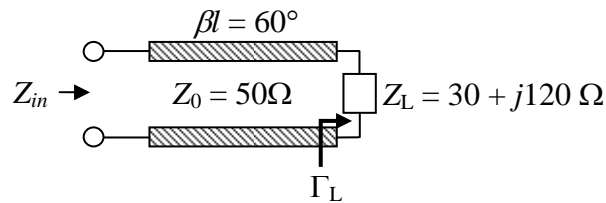



1. (30%) Locate the points in the Smith chart if $Z_0 = 50 \Omega$ for the following loads:
 (a) $Z_L = 50 \Omega$, (b) $Z_L = 100 + j60 \Omega$, (c) $Y_L = 0.012 + j0.016 \text{ S}$.
2. (20%) On the Smith Chart, please plot \bar{z}_L , \bar{z}_{in} , $|\Gamma_L|$, and $\angle \Gamma_L$.

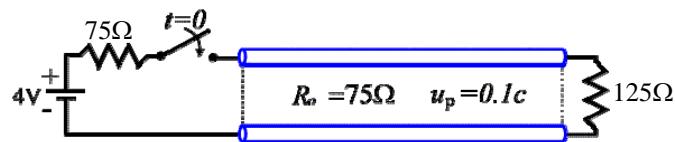

3. (10%) A step change in voltage propagates along a section of transmission line. Please derive voltage at the middle of transmission line after a long enough time (the reflections is settle down).



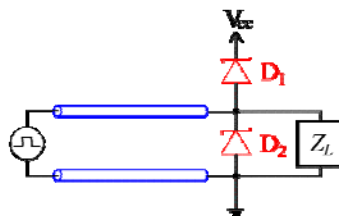4. (20%) In order to improve high-frequency performance in digital interconnects, a pair of Schottky diodes are often placed at load end of a transmission line. Please explain the purpose of diode D_1 and D_2 .



5. (20%) Design the open-ended shunt-stub matching network to match a load $Z_L = 70 + j110 \Omega$ to a $50\text{-}\Omega$ impedance transmission line. Please obtain lengths l and d .

