

General Physics II:

HW 6

Due on 4/23/2020

HW6-1: Problem 25-92 and 25-93 in Giancoli ([pp. 782](#)) (pp. 676)

HW6-2: Problem 26-36 in Giancoli ([pp. 810](#)) (pp. 702)

HW6-3: Problem 26-51 and 26-52 in Giancoli ([pp. 812](#)) (pp. 703)

HW6-1:

A. (prob. 25-92) For the wire in Fig. 25–39, whose diameter varies uniformly from a to b as shown, suppose a current $I = 2.0A$ enters at a . If $a = 2.5mm$ and $b = 4.0mm$, what is the current density (assume uniform) at each end?

B. (prob. 25-93) The cross section of a portion of wire increases uniformly as shown in Fig. 25–39, so it has the shape of a truncated cone. The diameter at one end is a and at the other it is b , and the total length along the axis is l . If the material has resistivity ρ , determine the resistance R between the two ends in terms of a , b , l , and ρ . Assume that the current flows uniformly through each section, and that the taper is small, i.e., $(b-a) \ll l$.


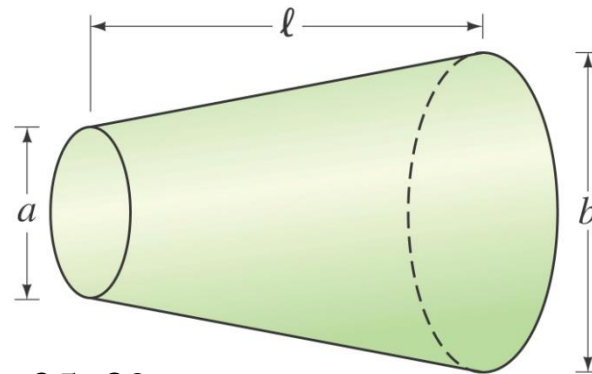
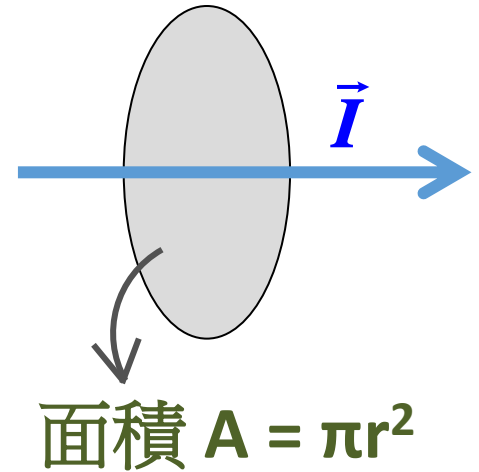


Fig. 25–39


(prob. 25-92)

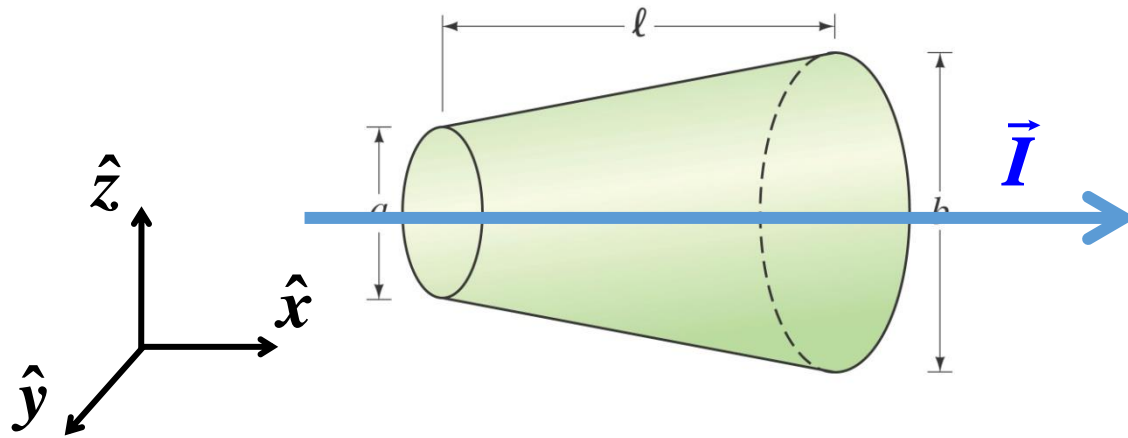

$$\vec{J}_a = \frac{\vec{I}}{A_a} = \frac{\vec{I}}{\pi \left(\frac{a}{2} \right)^2} = \frac{2.0 A}{\pi \left(\frac{2.5 \times 10^{-3}}{2} m \right)^2} \hat{x} = 4.07 \times 10^5 \hat{x} \text{ A / m}^2$$


$$\vec{J}_b = \frac{\vec{I}}{A_b} = \frac{\vec{I}}{\pi \left(\frac{b}{2} \right)^2} = \frac{2.0 A}{\pi \left(\frac{4.0 \times 10^{-3}}{2} m \right)^2} \hat{x} = 1.59 \times 10^5 \hat{x} \text{ A / m}^2$$

(prob. 25-93)

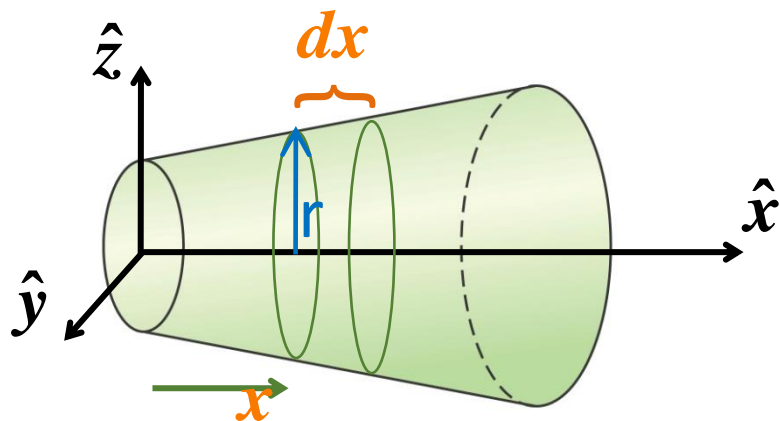

$$R = \rho \frac{L}{A}$$
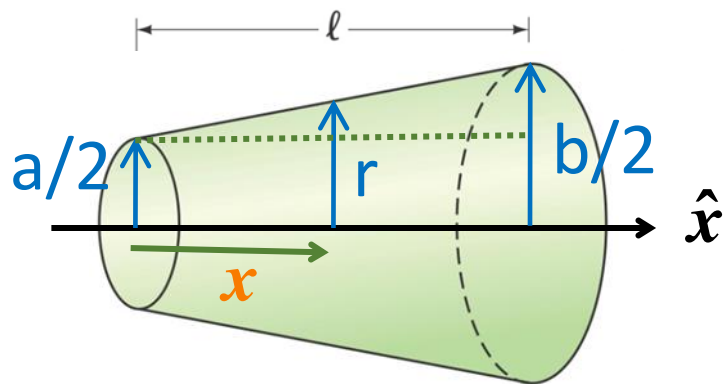
$$\Rightarrow dR = \rho \frac{dL}{A} = \rho \frac{dx}{\pi r^2}$$



$$r = \frac{a}{2} + \frac{x}{l} \left[\frac{(b-a)}{2} \right]$$

$$= \frac{al + bx - ax}{2l}$$

$$dR = \rho \frac{dx}{\pi r^2} = \rho \frac{dx}{\pi \left(\frac{al + bx - ax}{2l} \right)^2}$$

$$= \frac{4\rho l^2}{\pi} [al + (b-a)x]^{-2} dx$$


$$R = \int dR = \int_0^l \frac{4\rho l^2}{\pi} [al + (b-a)x]^{-2} dx$$

$$= \frac{4\rho l^2}{\pi} \left[-\frac{1}{b-a} \frac{1}{al + (b-a)x} \right]_0^l$$

$$= \frac{4\rho l^2}{\pi} \frac{-1}{b-a} \left[\frac{1}{bl} - \frac{1}{al} \right] = \frac{4\rho l}{\pi} \frac{1}{a-b} \frac{a-b}{ab} = \frac{4\rho l}{\pi ab}$$

Solution HW6-2:

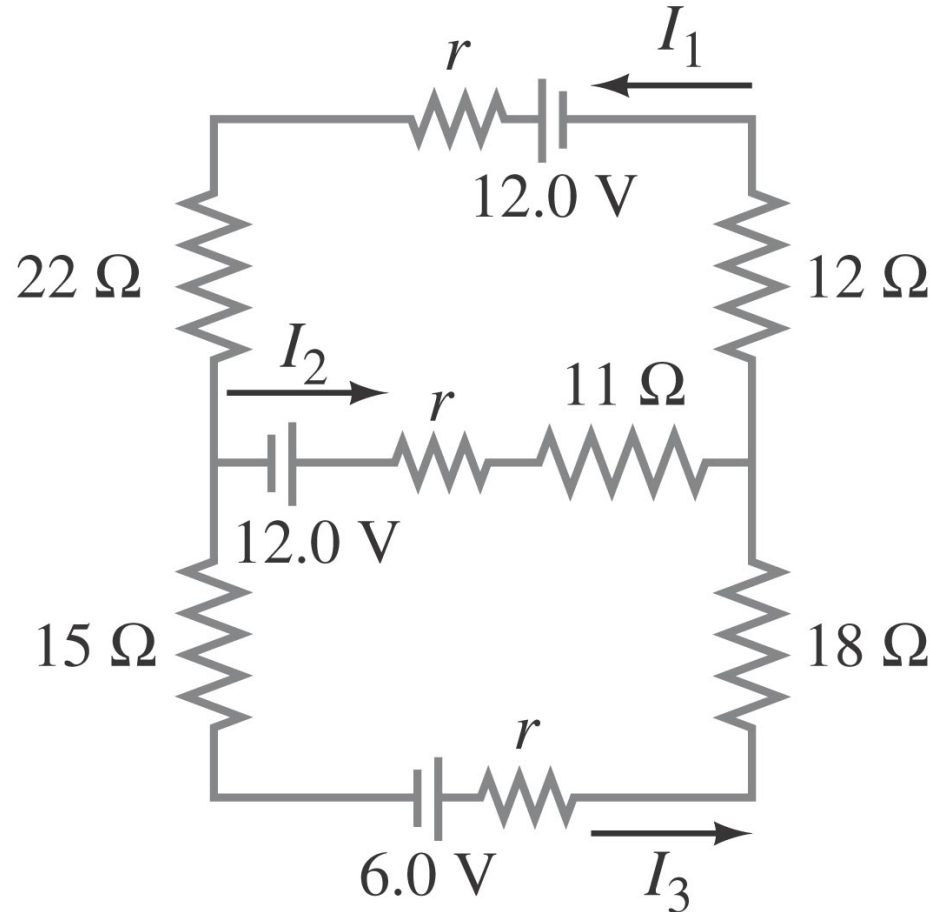- (a) Determine the currents I_1 , I_2 and I_3 in Fig.26-53. Assume the internal resistance of each battery is $r = 1.0\ \Omega$.
- (b) What is the terminal voltage of the 6.0-V battery?




Copyright © 2008 Pearson Education, Inc.

Fig.26-53

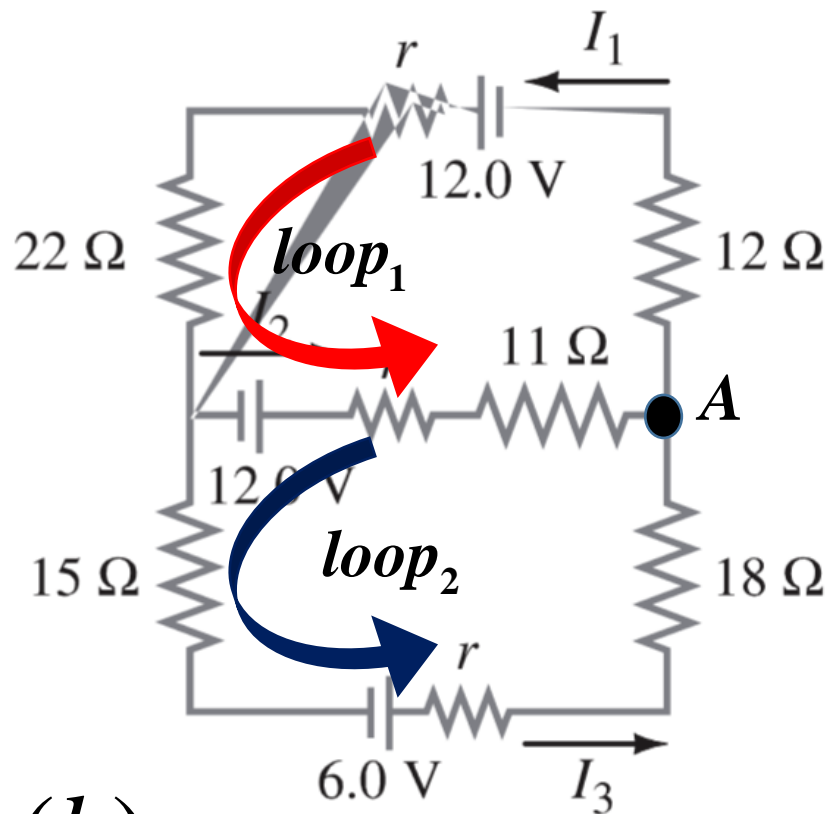(a) We get three equations in Fig.26-53 by Kirchhoff Circuit Laws :

$$\begin{cases} A \\ \text{loop}_1 \\ \text{loop}_2 \end{cases} \Rightarrow \begin{cases} I_1 = I_2 + I_3 \\ 24 - I_1(1 + 22 + 12) - I_2(1 + 11) = 0 \\ -6 - I_3(15 + 1 + 18) + I_2(11 + 1) = 0 \end{cases}$$



$$\Rightarrow \begin{cases} 35I_3 + 47I_2 = 24 \\ 34I_3 - 12I_2 = -6 \end{cases} \Rightarrow 2018I_2 = 1026$$

$$\Rightarrow \begin{cases} I_3 = \frac{3}{1009} \text{ (A)} \\ I_2 = \frac{513}{1009} \text{ (A)} \\ I_1 = \frac{516}{1009} \text{ (A)} \end{cases}$$

(b) $V = 6 - 1I_3 \approx 5.997 \text{ V}$

Solution HW6-3:

A. (prob. 26-51) Two resistors and two uncharged capacitors are arranged as shown in Fig. 26–62. Then a potential difference of **24V** is applied across the combination as shown.

(a) What is the potential at point **a** with switch **S** open? (Let $V=0$ at the negative terminal of the source.)

(b) What is the potential at point **b** with the switch open?

(c) When the switch is closed, what is the final potential of point **b**?

(d) How much charge flows through the switch **S** after it is closed ?

B. (prob. 26-52) Suppose the switch **S** in Fig. 26–62 is closed. What is the time constant (or time constants) for charging the capacitors after the **24V** is applied?


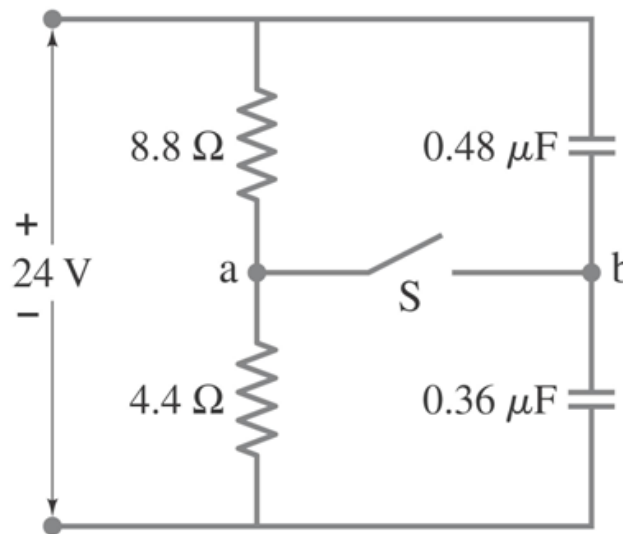


Fig. 26–62

(prob. 26-51)

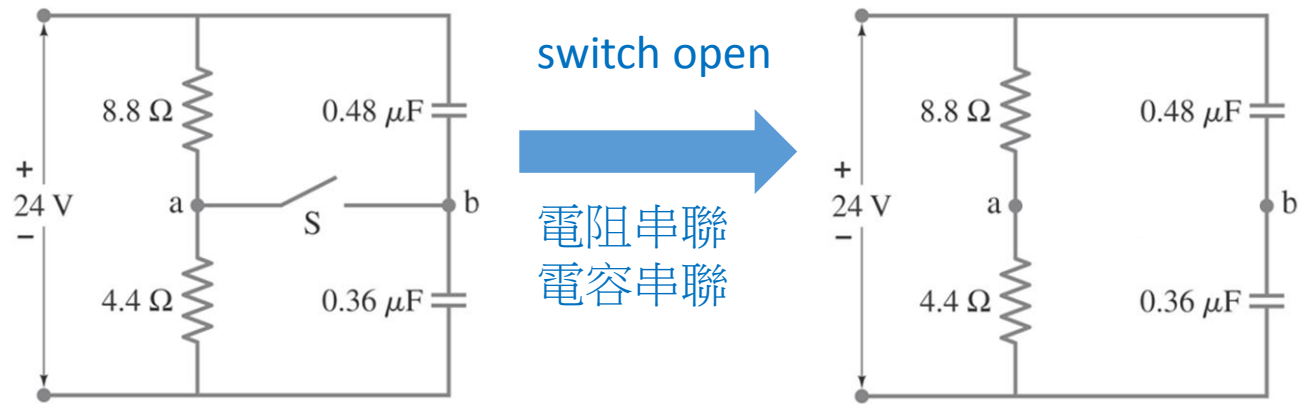

$$(a) \quad V_a = 24V - IR_1 = IR_2 = 24V \times \frac{R_2}{R_1 + R_2} = \mathbf{8V}$$

$$(b) \quad \text{串聯} : \frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow C = \frac{C_1 C_2}{C_1 + C_2} = \mathbf{0.2057 \mu F}$$

$$Q = VC = (24.0V)(0.2057 \mu F) = 4.937 \mu C = Q_1 = Q_2$$


$$V_b = 24V - \frac{Q_1}{C_1} = \frac{Q_2}{C_2} = \frac{4.937 \mu C}{0.2057 \mu F} = \mathbf{13.7V}$$

(c) 經過長時間，電容已充飽，電子便過不去 → 斷路
只剩下電阻那邊可走，回到(a)， $V_b = V_a = \mathbf{8V}$

$$(d) \quad Q = VC \Rightarrow \begin{cases} Q_1 = (16V)(0.48 \mu F) = 7.68 \mu C \\ Q_2 = (8V)(0.36 \mu F) = 2.88 \mu C \end{cases} \quad \text{電荷由b至a通過開關S}$$

$$Q = -7.68 \mu C + 2.88 \mu C = \mathbf{-4.8 \mu C}$$

(prob. 26-52)

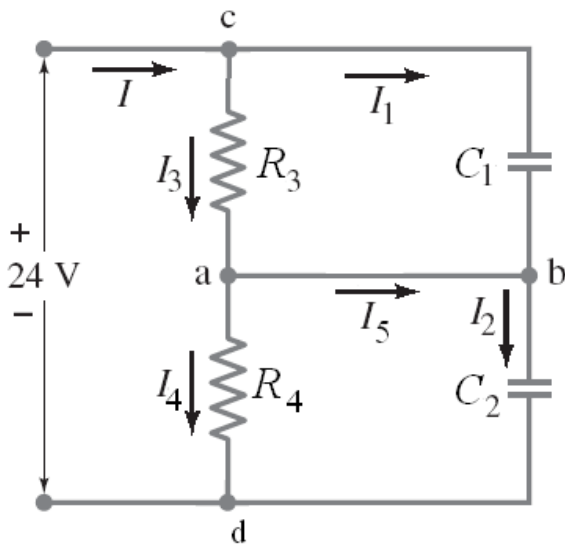

$$I = I_1 + I_3 \quad \dots\dots\dots(1)$$

$$I = I_2 + I_4 \quad \dots\dots\dots(2)$$

$$\varepsilon - \frac{Q_1}{C_1} - \frac{Q_2}{C_2} = 0 \quad \dots\dots\dots(3)$$

$$\frac{Q_1}{C_1} - I_3 R_3 = 0 \quad \dots\dots\dots(4)$$

$$\frac{Q_2}{C_2} - I_4 R_4 = 0 \quad \dots\dots\dots(5)$$

微分(3) : $\frac{d}{dt} \varepsilon - \frac{d}{dt} \frac{Q_1}{C_1} - \frac{d}{dt} \frac{Q_2}{C_2} = 0 \quad , \quad I = \frac{dQ}{dt}$

$$\Rightarrow 0 - \frac{I_1}{C_1} - \frac{I_2}{C_2} = 0 \Rightarrow I_2 = -I_1 \frac{C_2}{C_1}$$

代換(4)(5) : $I_3 = \frac{Q_1}{R_1 C_1} \quad , \quad I_4 = \frac{Q_2}{R_4 C_2}$

$$I_1 + I_3 = I_2 + I_4$$

$$I_1 + \frac{Q_1}{R_1 C_1} = -I_1 \frac{C_2}{C_1} + \frac{Q_2}{R_4 C_2} = -I_1 \frac{C_2}{C_1} + \frac{1}{R_4} \left(\varepsilon - \frac{Q_1}{C_1} \right)$$

$$\Rightarrow \varepsilon = I_1 R + \frac{Q_1}{C} = I_1 R_4 \left(\frac{C_1 + C_2}{C_1} \right) + Q_1 \left(\frac{R_4 + R_3}{R_3 C_1} \right)$$

$$\tau = RC$$

$$= R_4 \left(\frac{C_1 + C_2}{C_1} \right) \left(\frac{R_3 C_1}{R_4 + R_3} \right)$$

$$= \mathbf{2.5 \mu s}$$