

## Unit 13 Problem Solutions


- 13.2** Notice that this is a shift register. At each falling clock edge,  $Q_3$  takes on the value  $Q_2$  had right before the clock edge,  $Q_2$  takes on the value  $Q_1$  had right before the clock edge, and  $Q_1$  takes on the value  $X$  had right before the clock edge. For example, if the initial state is 000 and the input sequence is  $X = 1100$ , the state sequence is = 100, 110, 011, 001, and the output sequence is  $Z = (0)0011$ .  $Z$  is always  $Q_3$ , which does not depend on the present value of  $X$ . So it's a Moore machine. See FLD p. 758 for the state graph.

- 13.3 (a)**  $A^+ = AK_A' + A'J_A = A(B' + X) + A'(BX' + B'X)$   
 $B^+ = B'J_B + BK_B' = AB'X + B(A' + X')$   
 $Z = AB$

		$A^+$	
		$X$	
$AB$		0	1
00		0	1
01		1	0
11		0	1
10		1	1

		$B^+$	
		$X$	
$AB$		0	1
00		0	0
01		1	1
11		1	0
10		0	1

Present State $AB$	Next State $A^+B^+$		$Z$
	$X=0$	$X=1$	
00	00	10	0
01	11	01	0
11	01	10	1
10	10	11	0

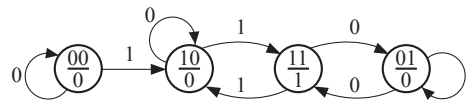

- 13.3 (b)**  $X = 0 \ 1 \ 1 \ 0 \ 0$   
 $AB = 00 \ 00 \ 10 \ 11 \ 01 \ 11$   
 $Z = (0) \ 0 \ 0 \ 1 \ 0 \ 1$

- 13.3 (c)** See FLD p. 758 for solution.

- 13.4 (a)**

		$X \ Q_1$			
		00	01	11	10
$Q_2 \ Q_3$					
00		0	0	0	0
01		0	0	0	0
11		0	0	0	0
10		1	1	1	1

$Q_1^+ = D_1$

		$X \ Q_1$			
		00	01	11	10
$Q_2 \ Q_3$					
00		0	0	0	0
01		1	1	1	1
11		1	1	1	1
10		0	0	0	0

$Q_2^+ = D_2$

		$X \ Q_1$			
		00	01	11	10
$Q_2 \ Q_3$					
00		1	1	1	1
01		1	1	1	1
11		0	0	1	1
10		0	0	1	1

$Q_3^+ = D_3$

		$X \ Q_1$			
		00	01	11	10
$Q_2 \ Q_3$					
00		0	0	1	1
01		0	0	1	1
11		1	1	0	0
10		1	1	0	0

$Z$

$Z$  depends on the input  $X$ , so this is a Mealy machine. Because there are more than 2 state variables, we cannot put the state table in Karnaugh Map order (i.e. 00, 01, 11, 10), but we can still read the next state and output from the Karnaugh map. For example, when the input is  $X = 1$  and the state is  $Q_1Q_2Q_3 = 110$ , we can read the next state and output from the  $XQ_1Q_2Q_3 = 1110$  position in the Karnaugh maps for  $Q_1^+$ ,  $Q_2^+$ ,  $Q_3^+$ , and  $Z$ . So in this case, the next state is  $Q_1^+Q_2^+Q_3^+ = 101$  and the output is  $Z = 0$ . The entire table can be derived from the Karnaugh maps in this manner. *Note:* We can also fill in the state table directly from the equations, without using Karnaugh maps. See FLD p. 758 for the state table and state graph.

- 13.4 (b - d)** See FLD p. 759 for solutions.

## Unit 13 Solutions

**13.5 (a)** Mealy machine, because the output,  $Z$ , depends on the input  $X$  as well as the present state.

**13.5 (c - d)** See FLD p. 759 for solutions.

**13.5 (b)**

		X A			
		00	01	11	10
B C	00	1	1	0	0
	01	1	1	0	0
	11	0	0	1	1
	10	0	0	1	1

*Note:* Not all Karnaugh map entries are needed. See FLD p. 759 for the state table.

**13.6 (a)** After a rising clock edge, it takes 4 ns for the flip-flop outputs to change. Then the ROM will take 8 ns to respond to the new flip-flop outputs. The ROM outputs must be correct at the flip-flop inputs for at least the setup time of 2 ns before the next rising clock edge. So the minimum clock period is  $(4 + 8 + 2)$  ns = 14 ns.

**13.6 (b)** The correct output sequence is 0101. See FLD p. 760 for the timing diagram.

**13.6 (c)** Read the state transition table from ROM truth table. See FLD p. 760 for the state graph and table.


Present State $Q_1 Q_2$	Next State $Q_1^+ Q_2^+$		Z	
	$X=0$	$X=1$	$X=0$	$X=1$
00	10	10	0	0
01	00	11	0	0
10	11	01	0	1
11	01	11	1	1

Alternate solution: Using Karnaugh map order, swap states  $S_2$  and  $S_3$  in the graph and table.


**13.7 (a)**  $Q_1^+ = J_1 Q_1' + K_1' Q_1 = X Q_1' + X Q_2' Q_1$   
 $Q_2^+ = J_2 Q_2' + K_2' Q_2 = X Q_2' + X Q_1 Q_2$   
 $Z = X' Q_2' + X Q_2$

Present State $Q_1 Q_2$	Next State $Q_1^+ Q_2^+$		Z	
	$X=0$	$X=1$	$X=0$	$X=1$
00	00	11	1	0
01	00	10	0	1
11	00	01	0	1
10	00	11	1	0

**13.7 (c)**  $Z = 00011$

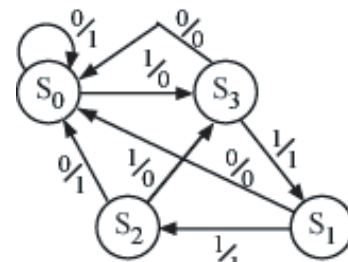



**13.7 (b)**

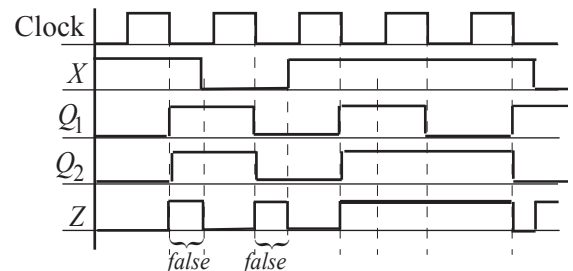

## Unit 13 Solutions

**13.8 (a)**  $Q_1^+ = J_1 Q_1' + K_1' Q_1 = X Q_2' Q_1' + X' Q_1$   
 $Q_2^+ = J_2 Q_2' + K_2' Q_2 = X Q_1 Q_2' + X' Q_2$   
 $Z = X Q_2' + X' Q_2$


Present State $Q_1 Q_2$	Next State $Q_1^+ Q_2^+$		Z	
	$X=0$	$X=1$	$X=0$	$X=1$
00	00	10	0	1
01	01	00	1	0
11	11	00	1	0
10	10	01	0	1

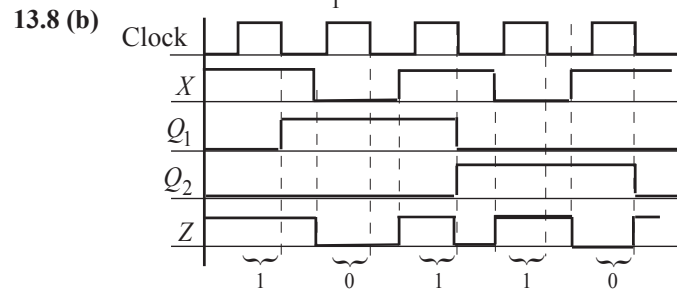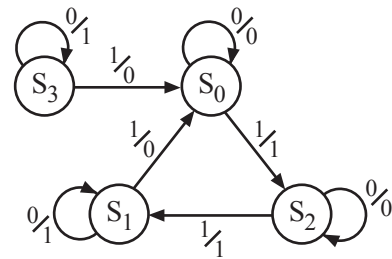


**13.8 (c)**  $Z = 10110$

**13.9 (a)**  $Q_1^+ = D_1 = (X_1' + X_2' + Q_1)(Q_1 + Q_2)(X_1' + Q_2)$   
 $Q_2^+ = D_2 = (X_1' X_2' + Q_1')(X_1 X_2 + Q_2)$   
 $Z = Q_1 Q_2'$

State	Present State $Q_1 Q_2$	Next State $X_1 X_2$				Z
		00	01	11	10	
$S_0$	00	00	01	01	00	0
$S_1$	01	11	11	01	11	0
$S_3$	11	11	10	10	10	0
$S_2$	10	10	10	00	00	1

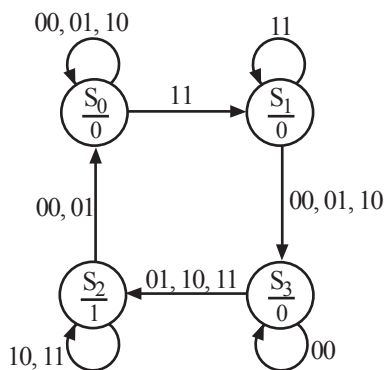


**13.9 (b)**

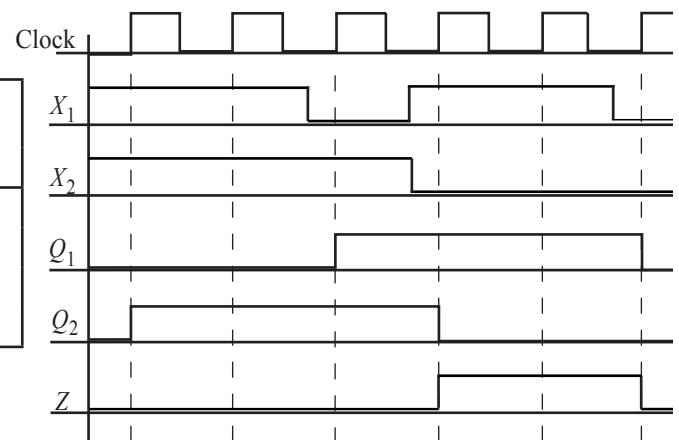

**13.9 (c)**  $Z = (0)000110$


**13.10(a)**  $Q_1^+ = D_1 = X_1 X_2 Q_1 + Q_1 Q_2 + X_2 Q_2$   
 $Q_2^+ = D_2 = (X_1' + X_2') Q_2 + (X_1 + X_2) Q_1'$   
 $Z = Q_1 Q_2'$

State	Present State $Q_1 Q_2$	Next State $X_1 X_2 =$				Z
		00	01	11	10	
$S_0$	00	00	01	01	01	0
$S_1$	01	01	11	11	01	0
$S_3$	11	11	11	10	11	0
$S_2$	10	00	00	10	00	1

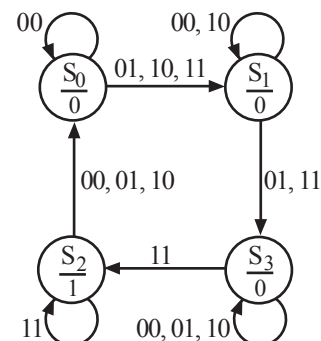

## Unit 13 Solutions

13.10(b)

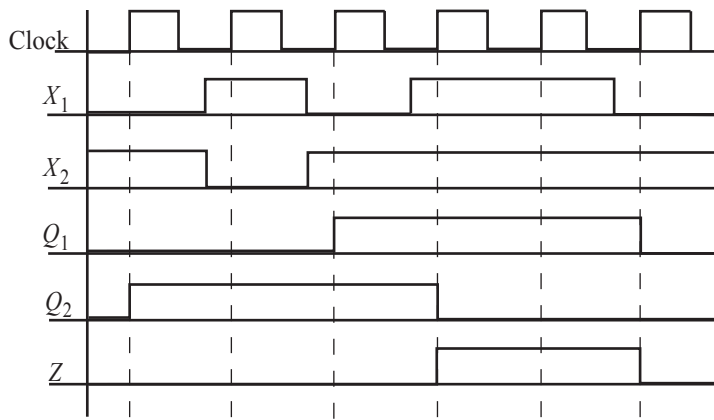

13.10(c)

Z = (0)000110

13.11 (a) Notice that Z depends on the input X, so this is a Mealy machine.

$$Q_1^+ = J_1 Q_1' + K_1' Q_1 = X Q_1' Q_2 + X' Q_1$$

$$Q_2^+ = J_2 Q_2' + K_2' Q_2 = X Q_1' Q_2' + X' Q_2$$

$$Z = Q_2 \oplus X = X Q_2' + X' Q_2$$

State	Present State $Q_1 Q_2$	Next State $Q_1^+ Q_2^+$		Z	
		X=0	X=1	X=0	X=1
S <sub>0</sub>	00	00	01	0	1
S <sub>1</sub>	01	01	10	1	0
S <sub>2</sub>	11	11	00	1	0
S <sub>3</sub>	10	10	00	0	1

Q <sub>1</sub> Q <sub>2</sub>		X	
		0	1
00	Q <sub>1</sub> <sup>+</sup>	0	0
01		0	1
11		1	0
10		1	0


Q <sub>1</sub> Q <sub>2</sub>		X	
		0	1
00	Q <sub>2</sub> <sup>+</sup>	0	1
01		1	0
11		1	0
10		0	0


Q <sub>1</sub> Q <sub>2</sub>		X	
		0	1
00	Z	0	1
01		1	0
11		1	0
10		0	1

Alternate solution: Swap states S<sub>2</sub> and S<sub>3</sub>.

13.11 (a)  
(cont.)

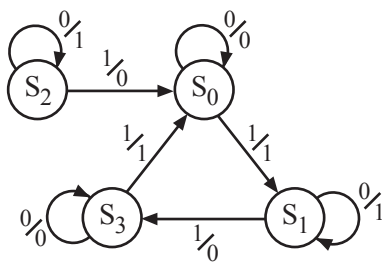

13.11  
(b)

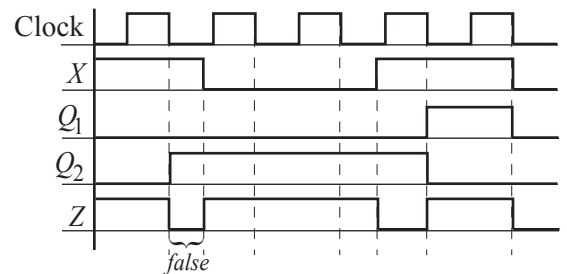

Correct output: Z = 11101

13.12(a) Notice that Z does not depend on either input, so this is a Moore machine.

$$Q_1^+ = X_1 X_2 Q_1 + Q_1 Q_2 + X_1' Q_2$$

$$Q_2^+ = Q_1' (X_1 + X_2) + Q_2 (X_1' + X_2')$$

$$= X_1' Q_1' + X_2 Q_1' + X_1' Q_2 + X_2' Q_2$$

$$Z = Q_1 Q_2'$$

Q <sub>2</sub>	Q <sub>1</sub>	
	0	1
0	0	1
1	0	0

Z

Q <sub>1</sub> Q <sub>2</sub>		X <sub>1</sub> X <sub>2</sub>			
		00	01	11	10
00	Q <sub>1</sub> <sup>+</sup>	0	0	0	0
01		0	0	1	1
11		1	1	1	1
10		0	0	1	0


  

Q <sub>1</sub> Q <sub>2</sub>		X <sub>1</sub> X <sub>2</sub>			
		00	01	11	10
00	Q <sub>2</sub> <sup>+</sup>	0	1	1	1
01		1	1	1	1
11		1	1	0	1
10		0	0	0	0


## Unit 13 Solutions

13.12(a)  
(cont.)

State	Present State $Q_1 Q_2$	Next State $X_1 X_2 =$				Z
		00	01	11	10	
$S_0$	00	00	01	01	01	0
$S_1$	01	01	01	11	11	0
$S_2$	11	11	11	10	11	0
$S_3$	10	00	00	10	00	1

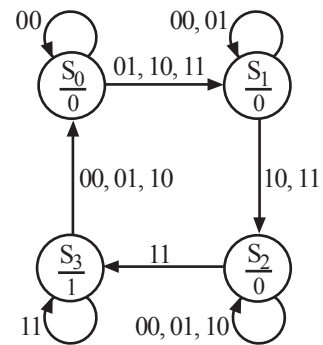


13.12(b)

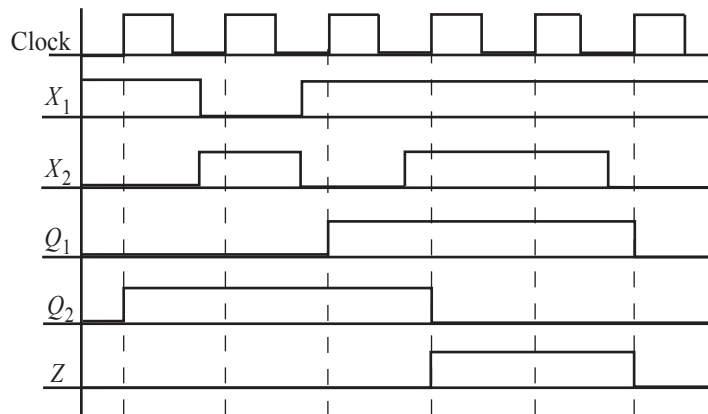


Correct output:  $Z = (0)00110$

13.13

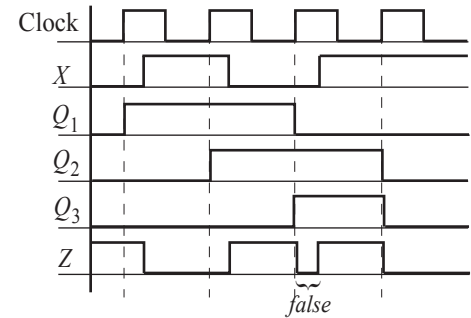

Correct output:  $Z = 1011$

13.14

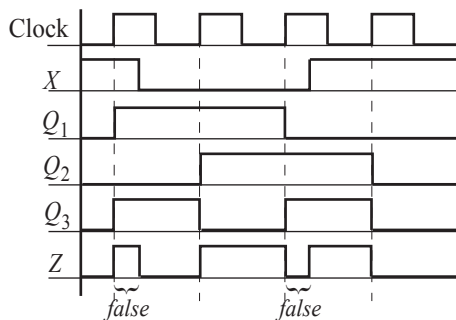

Correct output:  $Z = 0011$

13.15 (a)

$Q_2 Q_3$	$X Q_1$			
	00	01	11	10
00	0	0	0	1
01	0	0	0	1
11	0	0	0	1
10	1	1	1	1

$$D_1 = Q_1^+$$

$Q_2 Q_3$	$X Q_1$			
	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	1	1	1	1
10	1	1	0	0

$$D_2 = Q_2^+$$

$Q_2 Q_3$	$X Q_1$			
	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	0	0	1	1
10	0	0	1	1

$$D_3 = Q_3^+$$


$Q_2 Q_3$	$X Q_1$			
	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	1	1	0	0
10	1	1	0	0

$$Z$$


## Unit 13 Solutions

### 13.15 (a) (cont.)

State	Present State $Q_1Q_2Q_3$	Next State $Q_1^+Q_2^+Q_3^+$		Z	
		$X=0$	$X=1$	$X=0$	$X=1$
$S_0$	000	001	101	0	1
$S_1$	001	011	111	0	1
$S_2$	010	110	101	1	0
$S_3$	011	010	111	1	0
$S_4$	100	001	001	0	1
$S_5$	101	011	011	0	1
$S_6$	110	110	101	1	0
$S_7$	111	010	011	1	0

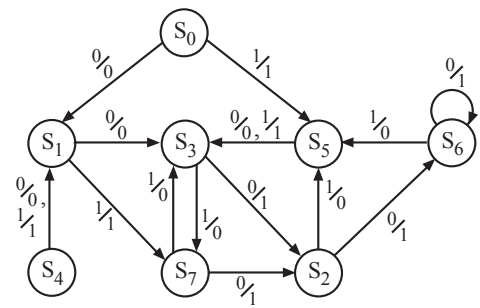

### 13.15 (b)

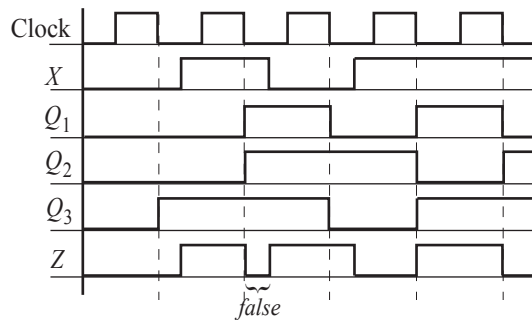

### 13.15 (c) From diagram: 0, 1, (0), 1, 0, 1

From graph: 0, 1, 1, 0, 1

(they are the same, except for the false output)

### 13.15 (d) Change the input on the falling edge of the clock (assuming negligible circuit delays).

### 13.16 (a)

$Q_2 Q_3 \backslash X Q_1$					
		00	01	11	10
$Q_2 Q_3$	00	1	1	0	0
	01	0	0	0	0
	11	0	0	0	0
	10	1	1	0	0

$$D_1 = Q_1^+$$

$Q_2 Q_3 \backslash X Q_1$		00	01	11	10
		00	01	11	10
$Q_2 Q_3$	00	0	1	1	1
	01	0	0	1	1
	11	0	0	0	0
	10	0	1	1	0

$$D_2 = Q_2^+$$


$Q_2 Q_3$		$X Q_1$			
		00	01	11	10
$Q_2 Q_3$	00	0	0	1	1
	01	0	0	1	1
	11	0	1	1	0
	10	0	1	1	0

$$D_3 = Q_3^+$$

$Q_2 Q_3$ \ $X Q_1$		00	01	11	10
		00	01	11	10
$Q_2 Q_3$	00	1	1	0	0
	01	0	0	1	1
	11	0	0	1	1
	10	1	1	0	0


$$Z$$

State	Present State $Q_1Q_2Q_3$	Next State $Q_1^+Q_2^+Q_3^+$		Z	
		$X=0$	$X=1$	$X=0$	$X=1$
$S_0$	000	100	011	1	0
$S_1$	001	000	011	0	1
$S_2$	010	100	000	1	0
$S_3$	011	000	000	0	1
$S_4$	100	110	011	1	0
$S_5$	101	000	011	0	1
$S_6$	110	111	011	1	0
$S_7$	111	001	001	0	1

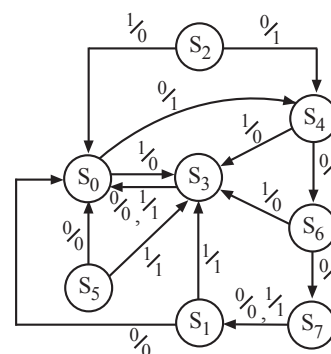

## Unit 13 Solutions

### 13.16 (b)

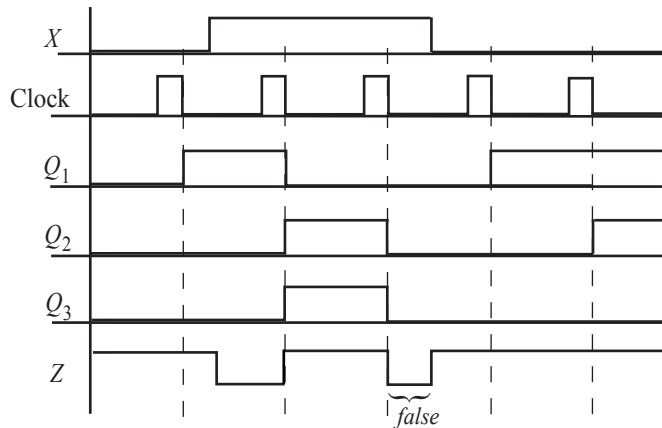

### 13.16 (c)

From diagram: 1 0 1 (0) 1 1

From graph: 1 0 1 1 1


(they are the same, except for the false output)

### 13.16 (d)

Change the input on the falling edge of the clock (assuming negligible circuit delays).


### 13.17 (a) Circuit 1

$Q_2Q_1Q_0$	Present State	Next State $X=0$	Next State $X=1$	Output $Z$
000	$S_0$	001	011	0
001	$S_1$	101	101	0
010	$S_2$	001	011	0
011	$S_3$	101	111	0
100	$S_4$	000	000	0
101	$S_5$	000	000	0
110	$S_6$	000	000	1
111	$S_7$	000	000	1

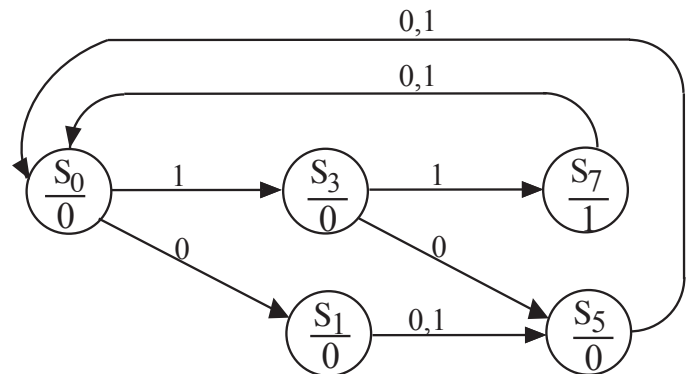

### Circuit 2

$Q_2Q_1Q_0$	Present State	Next State $X=0$	Next State $X=1$	Output $Z$
000	$S_0$	001	011	0
001	$S_1$	101	101	0
010	$S_2$	001	011	1
011	$S_3$	101	111	0
100	$S_4$	000	010	0
101	$S_5$	000	000	0
110	$S_6$	010	010	1
111	$S_7$	010	010	0

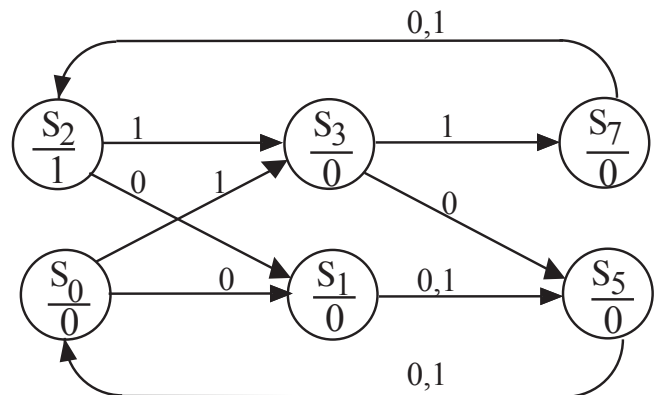

**13.17 (b)** Both circuits examine 3 consecutive inputs and produce an output of 1 if the three consecutive inputs represent a binary number larger than 5.

**13.17 (c)** The output of both circuits does not depend upon the input so they are Moore circuits.

**13.17 (d)** Circuit 1 produces the 1 output when the 3rd bit is present on the input, i.e., prior to the active clock edge when the 3rd bit is present. Circuit 2 produces the 1 output when the circuit enters the next state after receiving the 3rd bit. Circuit 1 has the functional dependence of a Moore circuit but the timing of a Mealy circuit. Circuit 2 is a Moore circuit both from the functional dependence and from the timing viewpoint.

## Unit 13 Solutions

13.18 (a)  $D_1 = Q_1' + Q_2$ ,  $D_2 = x$ ,  $z = Q_1 + Q_2'$

Present $Q_1Q_2$	Next $x = 0$	State $x = 1$	Output $z$
00	10	11	1
01	10	11	0
10	00	01	1
11	10	11	1

13.18 (d) Any input sequence ending with an odd number of 0's (1, 3, 5, etc.) followed by a single 1.

13.19 (a)  $D_1 = Q_1' + Q_2$ ,  $D_2 = xQ_2'$ ,  $z = Q_1 + Q_2'$

Present $Q_1Q_2$	Next $x = 0$	State $x = 1$	Output $z$
00	10	11	1
01	10	10	0
10	00	01	1
11	10	10	1


13.19 (d) Any sequence ending with an odd number of 0's (1, 3, 5, etc.) followed by an odd number of 1's.

13.20 (a)  $Q_1^+ = J_1Q_1' + K_1'Q_1$   
 $= (XQ_2' + XQ_2')Q_1' + (X + Q_2)Q_1$   
 $= XQ_1'Q_2' + X'Q_1'Q_2 + XQ_1 + Q_1Q_2'$   
 $= XQ_2' + X'Q_1'Q_2 + XQ_1 + Q_1Q_2'$   
 $Q_2^+ = J_2Q_2' + K_2'Q_2$   
 $= XQ_1'Q_2' + (X' + Q_1)Q_2$   
 $= XQ_1'Q_2' + X'Q_2 + Q_1Q_2$   
 $Z = Q_1Q_2$



Present State $Q_1Q_2$	Next State $Q_1^+Q_2^+$		$Z$
	$X = 0$	$X = 1$	
00	00	11	0
01	11	00	0
10	10	10	0
11	01	11	1

13.20 (c)  $Z = (0)01101$

13.18 (c)

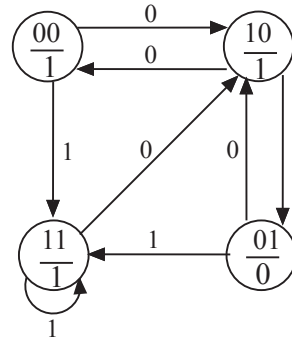


13.19 (c)

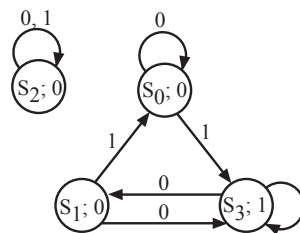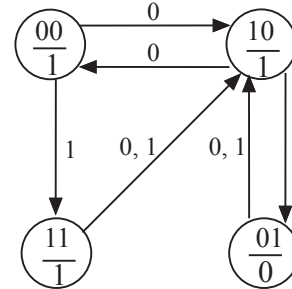

The circuit is a Moore circuit. State 2 is unused.

13.20 (b)

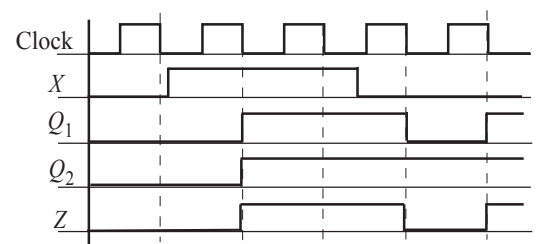




## Unit 13 Solutions

13.21

Clock Cycle	Information Gathered
1	$Q_1Q_2 = 00, X = 0 \Rightarrow Z = 1, Q_1^+Q_2^+ = 01$
2	$Q_1Q_2 = 01, X = 0 \Rightarrow Z = 0; X = 1 \Rightarrow Z = 1, Q_1^+Q_2^+ = 11$
3	$Q_1Q_2 = 11, X = 1 \Rightarrow Z = 1; X = 0 \Rightarrow Z = 0, Q_1^+Q_2^+ = 10$
4	$Q_1Q_2 = 10, X = 0 \Rightarrow Z = 1; X = 1 \Rightarrow Z = 0, Q_1^+Q_2^+ = 00$
5	$Q_1Q_2 = 00, X = 1 \Rightarrow Z = 0, Q_1^+Q_2^+ = 10$
6	$Q_1Q_2 = 10, X = 1 \Rightarrow (Z = 0); X = 0 \Rightarrow (Z = 1), Q_1^+Q_2^+ = 11$
7	$Q_1Q_2 = 11, X = 0 \Rightarrow (Z = 0); X = 1 \Rightarrow (Z = 1), Q_1^+Q_2^+ = 01$
8	$Q_1Q_2 = 01, X = 1 \Rightarrow (Z = 1); X = 0 \Rightarrow (Z = 0), Q_1^+Q_2^+ = 00$
9	$Q_1Q_2 = 00, X = 0 \Rightarrow (Z = 1)$

*Note:* Information inside parentheses was already obtained in a previous clock cycle.

Present State $Q_1Q_2$	Next State $Q_1^+Q_2^+$		Z	
	$X = 0$	$X = 1$	$X = 0$	$X = 1$
00	01	10	1	0
01	00	11	0	1
10	11	00	1	0
11	10	01	0	1

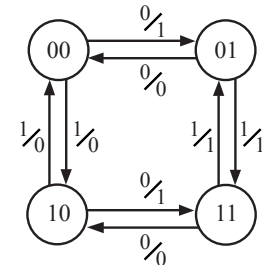


13.22

Clock Cycle	Information Gathered
1	$Q_1Q_2 = 00, X = 0 \Rightarrow Z = 0, Q_1^+Q_2^+ = 10$
2	$Q_1Q_2 = 10, X = 0 \Rightarrow Z = 1; X = 1 \Rightarrow Z = 0, Q_1^+Q_2^+ = 01$
3	$Q_1Q_2 = 01, X = 1 \Rightarrow Z = 0; X = 0 \Rightarrow Z = 1, Q_1^+Q_2^+ = 10$
4	$Q_1Q_2 = 10, X = 0 \Rightarrow (Z = 1), Q_1^+Q_2^+ = 11$
5	$Q_1Q_2 = 11, X = 0 \Rightarrow Z = 0, Q_1^+Q_2^+ = 11$
6	$Q_1Q_2 = 11, X = 0 \Rightarrow (Z = 0); X = 1 \Rightarrow Z = 1, Q_1^+Q_2^+ = 01$
7	$Q_1Q_2 = 01, X = 1 \Rightarrow (Z = 0), Q_1^+Q_2^+ = 00$
8	$Q_1Q_2 = 00, X = 1 \Rightarrow Z = 1, Q_1^+Q_2^+ = 11$
9	$Q_1Q_2 = 11, X = 1 \Rightarrow (Z = 1)$

*Note:* Information inside parentheses was already obtained in a previous clock cycle.

Present State $Q_1Q_2$	Next State $Q_1^+Q_2^+$		Z	
	$X = 0$	$X = 1$	$X = 0$	$X = 1$
00	10	11	0	1
01	10	00	1	0
10	11	01	1	0
11	11	01	0	1

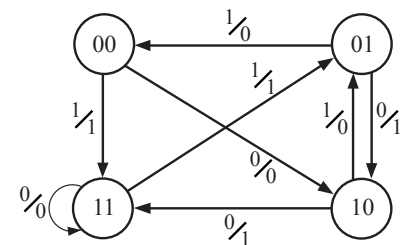

13.23

Clock Cycle	Information Gathered
1	$Q_1Q_2 = 00, X_1X_2 = 01 \Rightarrow Z_1Z_2 = 10, Q_1^+Q_2^+ = 01$
2	$Q_1Q_2 = 01, X_1X_2 = 01 \Rightarrow Z_1Z_2 = 01; X_1X_2 = 10 \Rightarrow Z_1Z_2 = 10, Q_1^+Q_2^+ = 10$
3	$Q_1Q_2 = 10, X_1X_2 = 10 \Rightarrow Z_1Z_2 = 00; X_1X_2 = 11 \Rightarrow Z_1Z_2 = 00, Q_1^+Q_2^+ = 01$
4	$Q_1Q_2 = 01, X_1X_2 = 11 \Rightarrow Z_1Z_2 = 11; X_1X_2 = 01 \Rightarrow (Z_1Z_2 = 01), Q_1^+Q_2^+ = 11$
5	$Q_1Q_2 = 11, X_1X_2 = 01 \Rightarrow Z_1Z_2 = 01$

*Note:* When  $Q_1Q_2 = 01$ , the outputs  $Z_1Z_2$  vary depending on the inputs  $X_1X_2$ , so this is a Mealy machine.

Present State $Q_1Q_2$	$Q_1^+Q_2^+$ $X_1X_2 =$				$Z_1Z_2$ $X_1X_2 =$			
	00	01	11	10	00	01	11	10
00	?	01	?	?	?	10	?	?
01	?	11	?	10	?	01	11	10
11	?	?	?	?	?	01	?	?
10	?	?	01	?	?	?	00	00


Unit 13 Solutions

13.24

Present State $Q_1Q_2$	$Q_1^+Q_2^+$ $X_1X_2=$				$Z_1Z_2$ $X_1X_2=$			
	00	01	11	10	00	01	11	10
00	?	01	?	?	?	10	?	?
01	?	11	?	10	?	01	11	10
11	?	?	?	?	?	01	?	?
10	?	?	01	?	?	?	00	00

? indicates next state or output values that cannot be determined from the timing chart

13.25(b)

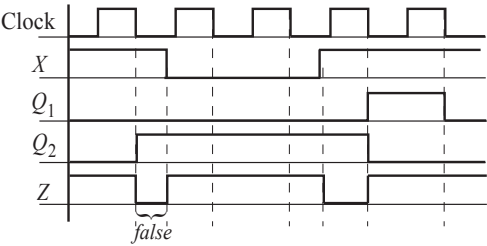


13.25(c) Z = 11101


13.25(a)

$Q_1^+ = D_1 = X'Q_1 + XQ_1'Q_2$   
 $Q_2^+ = D_2 = X'Q_2 + XQ_1'Q_2'$   
 $Z = X'Q_2 + XQ_1'Q_2' + XQ_1Q_2'$

Present State $Q_1Q_2$	Next State $Q_1^+Q_2^+$		Z	
	$X=0$	$X=1$	$X=0$	$X=1$
$S_0=00$	00	01	0	1
$S_1=01$	01	10	1	0
$S_3=11$	11	00	1	0
$S_2=10$	10	00	0	1

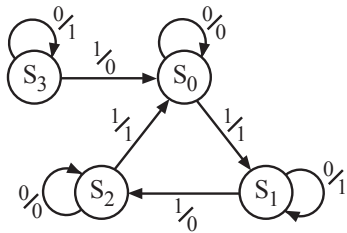


13.26 (a)

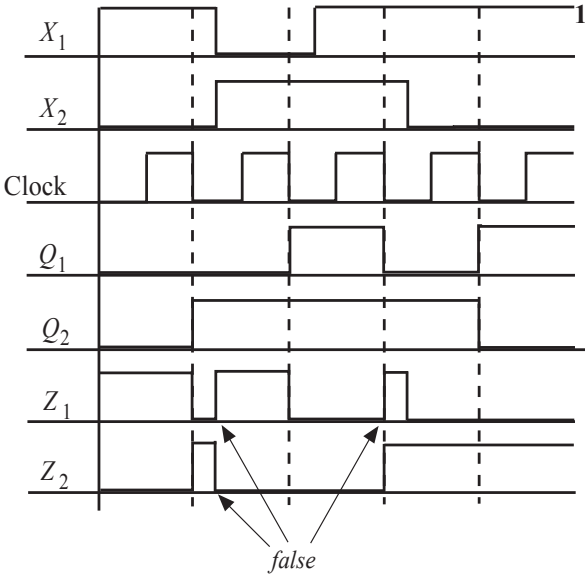

Correct output:  $Z_1Z_2 = 10, 10, 00, 01$

13.26 (b)


Present State $Q_1Q_2$	$Q_1^+Q_2^+$ $X_1X_2=$				$Z_1Z_2$ $X_1X_2=$			
	00	01	10	11	00	01	10	11
00	00	00	01	01	10	10	10	10
01	11	11	10	10	00	10	01	11
10	11	00	11	00	00	00	01	01
11	10	01	10	01	00	00	00	00

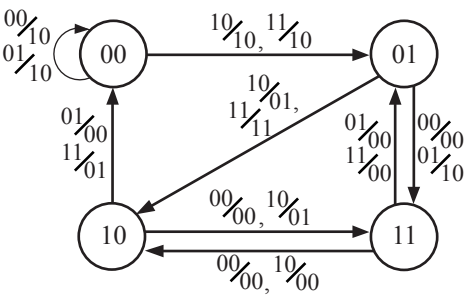

## Unit 13 Solutions


- 13.27** Transition table using a straight binary state assignment:

State	Present State $Q_1Q_2Q_3$	Next State $Q_1^+Q_2^+Q_3^+$		Z	
		$X=0$	$X=1$	$X=0$	$X=1$
$S_0$	000	001	011	0	0
$S_1$	001	010	011	0	0
$S_2$	010	001	011	0	1
$S_3$	011	100	000	0	0
$S_4$	100	011	000	0	1

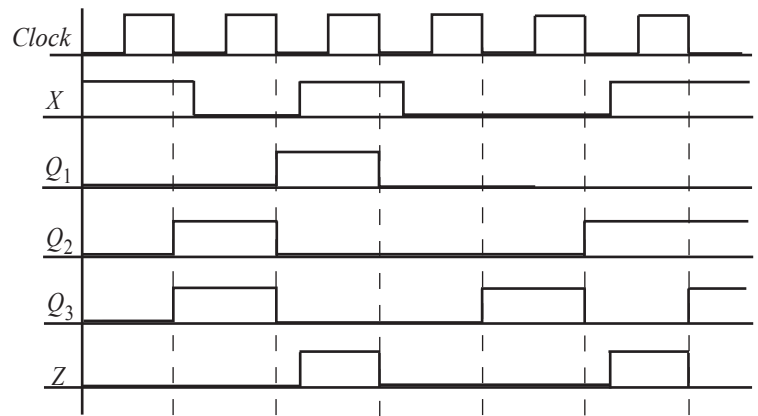

Correct output:  $Z = 0, 0, 1, 0, 0, 1$

- 13.28 (a)**

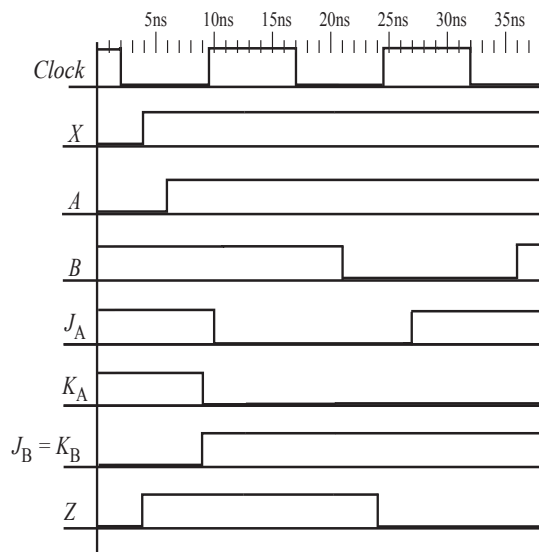


All flip-flop inputs are stable for more than the setup time before each falling clock edge. So the circuit is operating properly.

- 13.25(b)** If  $X$  is changed early enough:

Minimum clock period = Flip-flop propagation delay + Two NAND-gate delays + Setup time  
 $= 4 + (3 + 3) + 2 = 12 \text{ ns}$

$X$  can change as late as 8 ns (two NAND-gate delays plus the setup time) before the next falling edge without causing improper operation.

- 13.29**

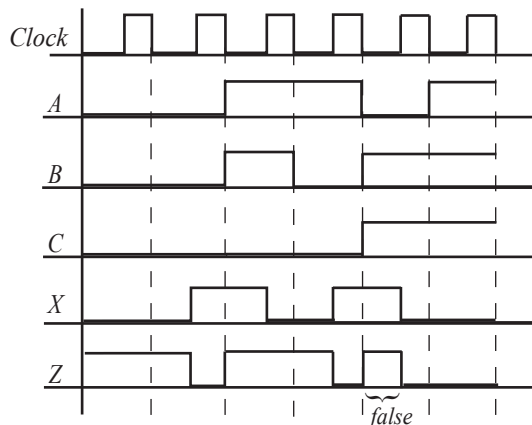

Correct output:  $Z = 1\ 0\ 1\ 0\ 1$

Deriving the State Table:

JK flip-flop equation:

$$Q^+ = JQ' + K'Q$$

$$\therefore A^+ = (X'C + XC')A' + X'A$$

$$[\text{As, } J_A = X'C + XC', K_A = X, Q = A]$$

$$= A'X'C + A'XC' + X'A$$

Similarly,  $B^+ = XC' + XA + X'A'C$

$$C^+ = 0' \cdot C + (XB'A) \cdot C' = C + XB'A$$

$$Z = XB + X'C' + X'B'A$$

## Unit 13 Solutions

### 13.29 (cont.)

$$A^+$$

BC \ XA	00	01	11	10
00	0	1	0	1
01	1	1	0	0
11	1	1	0	0
10	0	1	0	1

$$B^+$$

BC \ XA	00	01	11	10
00	0	0	1	1
01	1	0	1	0
11	1	0	1	0
10	0	0	1	1

$$C^+$$

BC \ XA	00	01	11	10
00	0	0	1	0
01	1	1	1	1
11	1	1	1	1
10	0	0	0	0

$$Z$$

BC \ XA	00	01	11	10
00	1	1	0	0
01	0	1	0	0
11	0	0	1	1
10	1	1	1	1

From the Karnaugh maps, we can get the state table that follows:

State	Present State <i>ABC</i>	Next State <i>A<sup>+</sup>B<sup>+</sup>C<sup>+</sup></i>		<i>Z</i>	
		<i>X=0</i>	<i>X=1</i>	<i>X=0</i>	<i>X=1</i>
<i>S</i> <sub>0</sub>	000	000	110	1	0
<i>S</i> <sub>1</sub>	001	111	001	0	0
<i>S</i> <sub>2</sub>	010	000	110	1	1
<i>S</i> <sub>3</sub>	011	111	001	0	1
<i>S</i> <sub>4</sub>	100	100	011	1	0
<i>S</i> <sub>5</sub>	101	101	011	1	0
<i>S</i> <sub>6</sub>	110	100	010	1	1
<i>S</i> <sub>7</sub>	111	101	011	0	1

### 13.30

$$R = X_2 (X_1' + B)$$

$$S = X_2' (X_1' + B')$$

$$A^+ = A[(X_2) (X_1' + B)]' + X_2' (X_1' + B')$$

$$= A (X_2' + X_1 B') + X_2' X_1' + X_2' B'$$

$$A^+ = AX_2' + AX_1 B' + X_2' X_1' + X_2' B'$$

$$T = X_1' B A + X_1' B' A'$$

$$B^+ = B T' + B' T$$

$$= B(X_1' B A + X_1' B' A')' B' (X_1' B A + X_1' B' A')$$

$$= B [(X_1' B A)' (X_1' B' A')'] + X_1' B' A'$$

$$= B [(X_1 + B' + A') (X_1 + B + A)] + X_1' B' A'$$

$$= (B X_1 + B A') (X_1 + B + A) + X_1' B' A'$$

$$= B X_1 + B X_1 + B X_1 A + B A' X_1 + B A' + X_1' B' A'$$

$$= X_1 B (1 + 1 + A + A') + A' (B + X_1' B)$$

$$= X_1 B + A' B + X_1' A'$$

### 13.30 (cont.)

State	Present State <i>AB</i>	<i>A<sup>+</sup>B<sup>+</sup></i> <i>X<sub>1</sub>X<sub>2</sub></i>				<i>Z<sub>1</sub>Z<sub>2</sub></i> <i>X<sub>1</sub>X<sub>2</sub></i>			
		00	01	10	11	00	01	10	11
<i>S</i> <sub>0</sub>	00	11	01	10	00	10	10	00	00
<i>S</i> <sub>1</sub>	01	11	01	01	01	11	00	11	00
<i>S</i> <sub>2</sub>	10	10	00	10	10	01	00	01	00
<i>S</i> <sub>3</sub>	11	10	00	11	01	00	00	00	00

