


Electromagnetic Wave

The Final Examination

6/7/2021 (Monday) 8:00 AM-12:00 PM

4 大題 , 總分 103 分 (+ 8 分 Bonus)

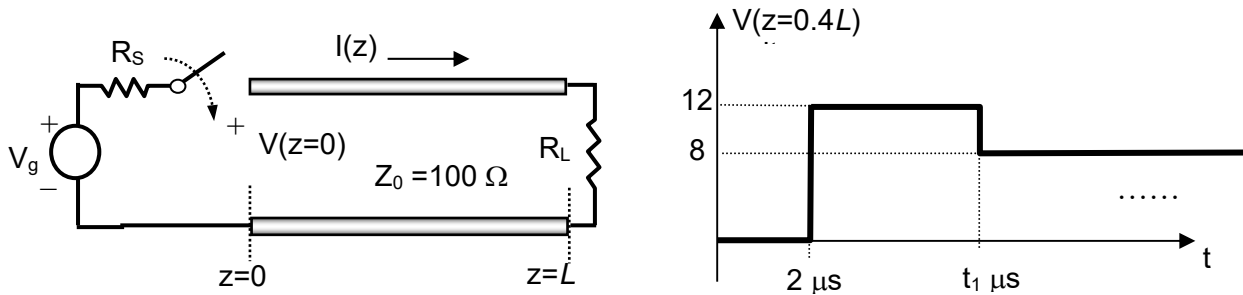
(37%) 1. A $100\text{-}\Omega$ TEM dielectric-filled ($\epsilon_r=9$) transmission line is excited by connecting it to the voltage source at $t = 0$ shown as below. The voltage $V(z = 0.4L, t)$ observed at the input of the line is given by :



- (3%) What is the propagation velocity v_p of this transmission line ?
- (3%) What is the length L of this line?
- (3%) Find t_1 where the voltage is changed.
- (3%) What is the reflection coefficient Γ_L ?
- (3%) What is the value of the load R_L ?
- (3%) What is the value of the load R_s ?
- (3%) What is the value of generator voltage V_g ?
- (6%) Draw the equivalent lump circuit model of this transmission line; find the value of the capacitance $C\ell$ and inductance $L\ell$ per meter ?
- (5%) Plot the bounce (Reflection) diagram (Time vs. z)
- (5%) Plot voltage vs. time observed at $z = 0.8L$ ($t=0 \sim 12\ \mu\text{s}$)


(18%) 2. A $50\text{-}\Omega$ transmission (3.65λ -long) is connected to a voltage generator that has an impedance of $50\ \Omega$. It's known that input impedance at $z=0$ (at generator) is $(10+j25)\ \Omega$.

- (3%) What is the voltage standing wave ratio on this line?
- (3%) What is the load impedance R_L ?
- (3%) What is the reflection coefficient at the load ? ($|\Gamma|e^{j\theta}$)
- (3%) How far is the first voltage minimum from the load ?
- (3%) How far is the first voltage maximum from the load ?
- (3%) What is the input impedance at the position $z=1.5\ \lambda$?

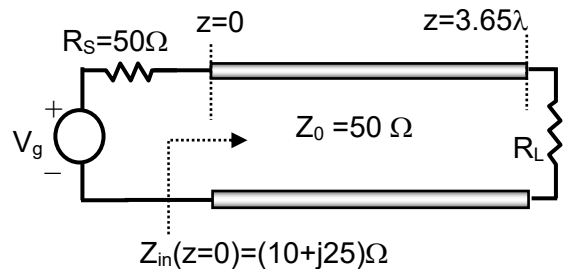

(18%) 3. The $50\text{-}\Omega$ transmission line is required to deliver equal power to two separated loads (Z_{L1} , Z_{L2}) which are connected in parallel. To accomplish this mission, only quarter-wavelength ($\lambda/4$) transformer can be used for impedance matching line. Assume that all lines are lossless, please answer the following questions:

- (3%) Find Z_L for 100% power delivering.
- (6%) Find Z_{in1} and Z_{in2} for equal power splitting
- (3%) For Z_{L1} , find the impedance R_1 of the inserted $\lambda/4$ transformer.
- (3%) Since Z_{L2} is NOT a pure resistance, find the minimum distance d that $\lambda/4$ transformer can be used for matching.
- (3%) Continue with (d), find the impedance R_2 of the inserted $\lambda/4$ transformer.

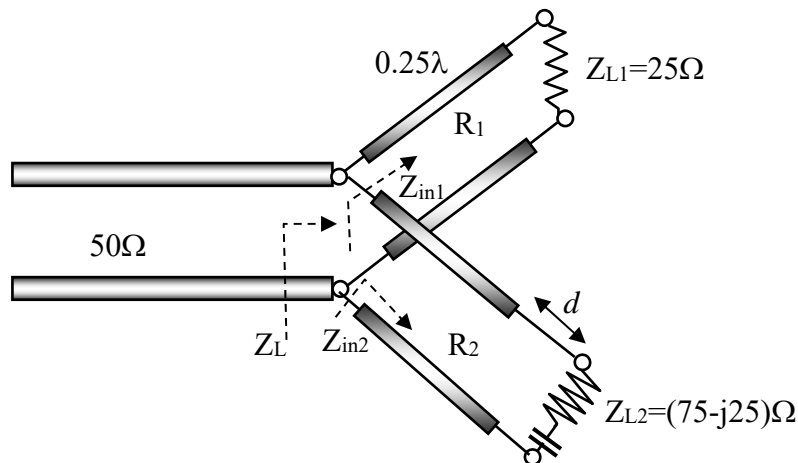

(30%) 4. A $50\text{-}\Omega$ transmission line is connected to a $(100 + j120)\text{-}\Omega$ load. Design the matching network based on the following methods.


- (20%) Design a double-stub matching network using a short circuited stub. Simply SKETCH the design procedure on the simplified Smith chart step by step. You need to provide both solutions.
- (10%) Sketch TWO kinds of matching network using lumped elements (L , C). At least two lumped elements are used (L -type、 π -type、 T -type、*ladder*-Type). Also sketch the simplified Smith chart to explain your design concept. (You don't need to find the element values)

(8%) 5. **Bonus**

- (4%) What is the advantage of the 4-element ladder-type over the 2-element L-type matching network ?
- (4%) What is the advantage of the double-stub matching network over the single-stub matching network ?


The Complete Smith Chart

Black Magic Design

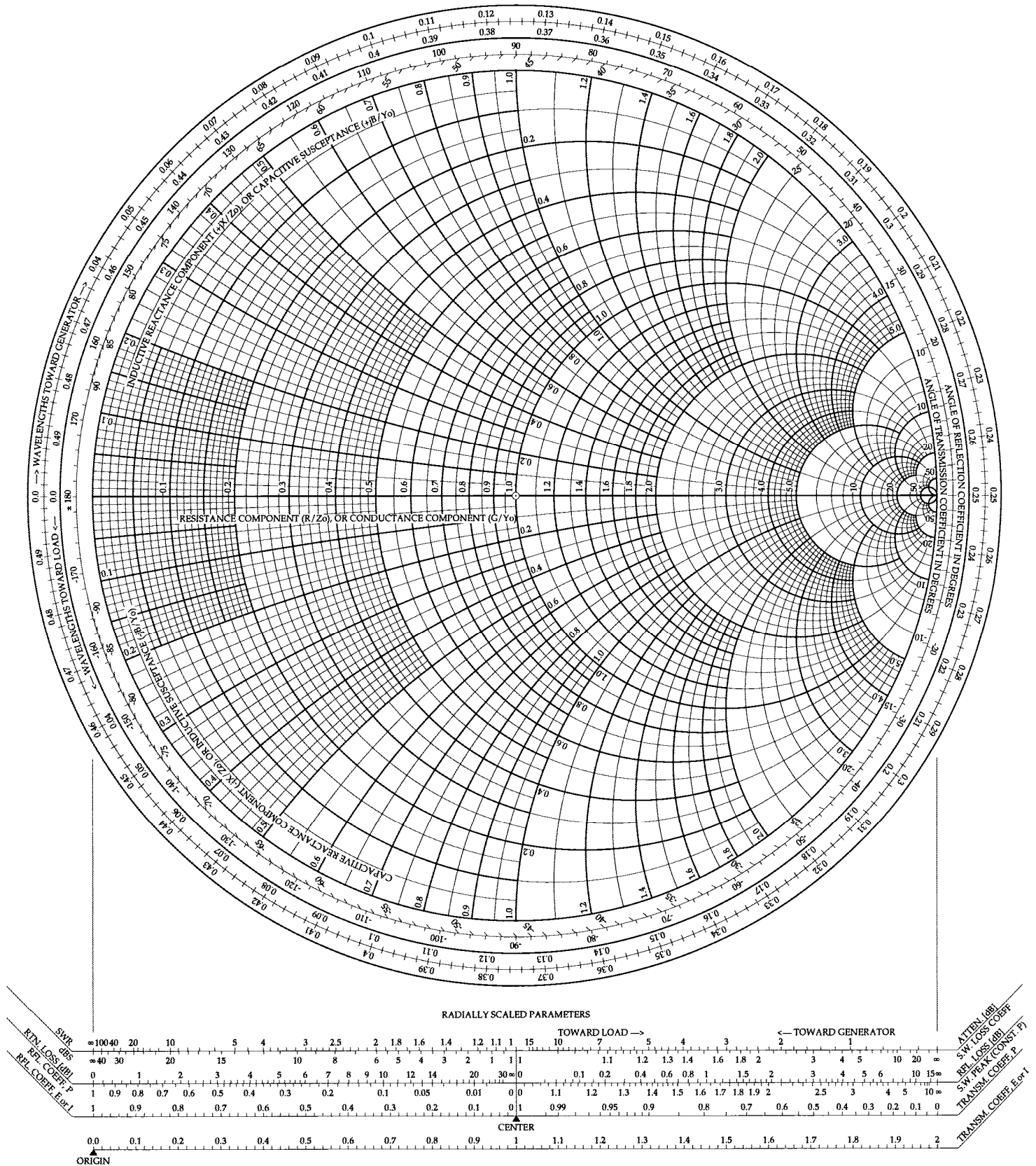

The Complete Smith Chart

Black Magic Design

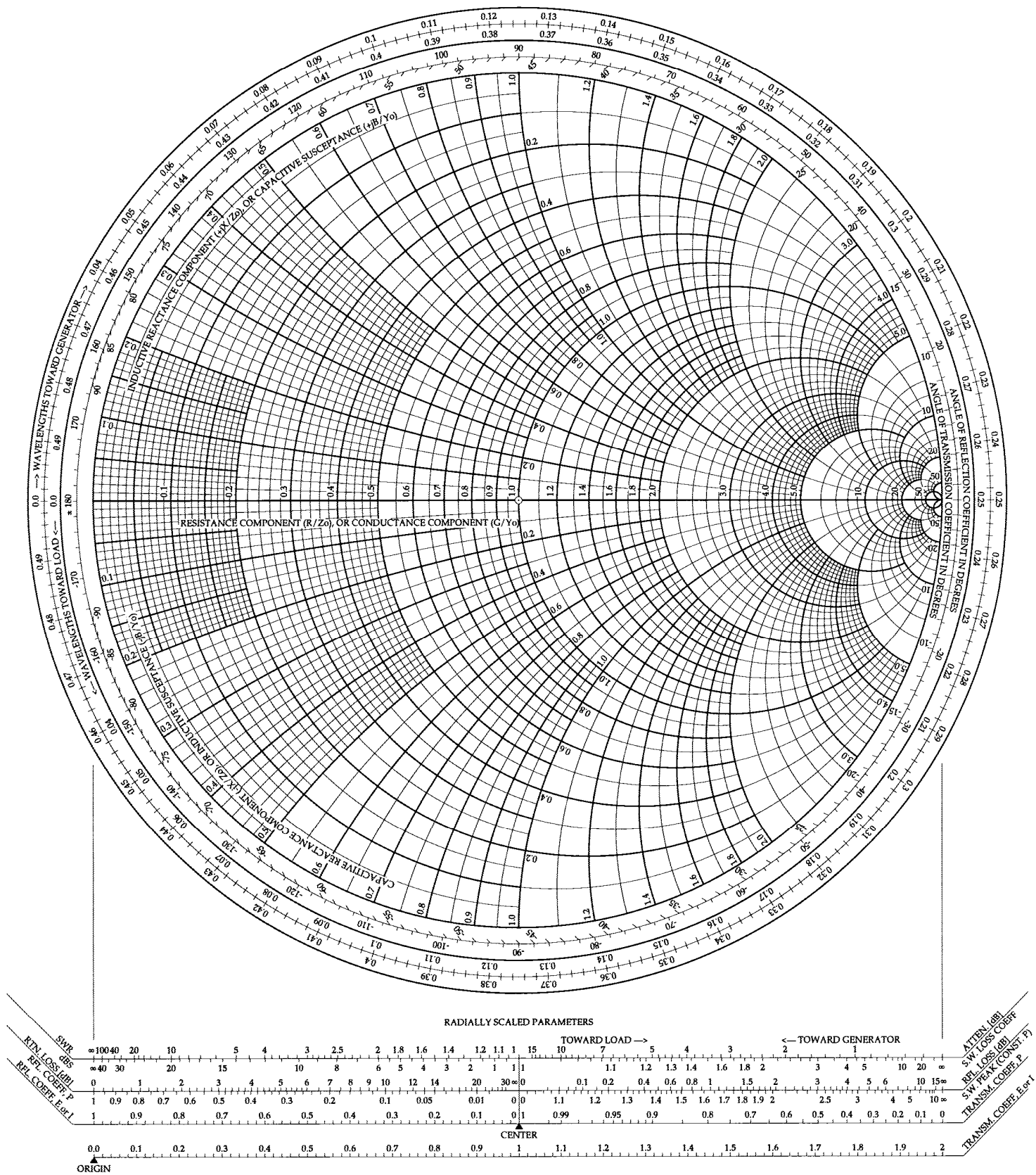

The Complete Smith Chart

Black Magic Design

