

GP(II).spring.2020  
HW11.solution

### HW11-1:

- (a) For the AC circuit shown in Fig. 1(a), given that  $I(t) = I_0 \cos(\omega t)$ , find the voltage  $V(t)$  for the circuit in Fig. 1(a) and  $|V_L/V|$  as a function of  $\omega$
- (b) For the AC circuit shown Fig. 1(b), given that  $V(t) = V_0 \cos(\omega t)$ , find the current  $I(t)$  and  $|I_C/I|$  as a function of  $\omega$ .

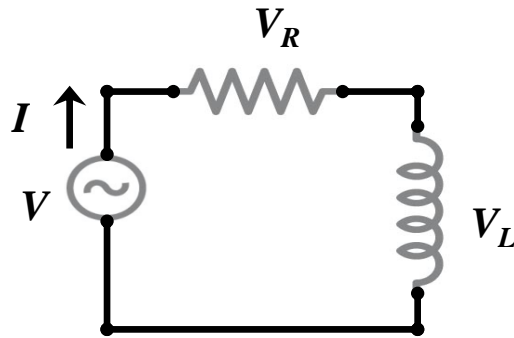


Fig. 1(a)

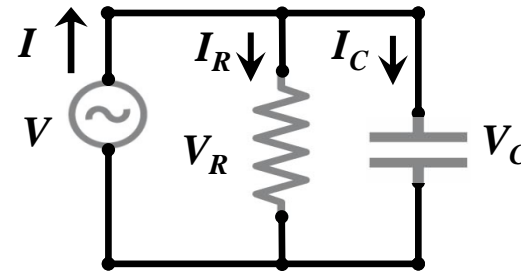


Fig. 1(b)


## Solution of HW12-1:

(a) RL 串聯  $\rightarrow$  電流  $I(t)$  一樣

$$V_R = IR = RI_0 \cos \omega t$$

$$V_L = L \frac{dI}{dt} = LI_0 (-\omega \sin \omega t)$$
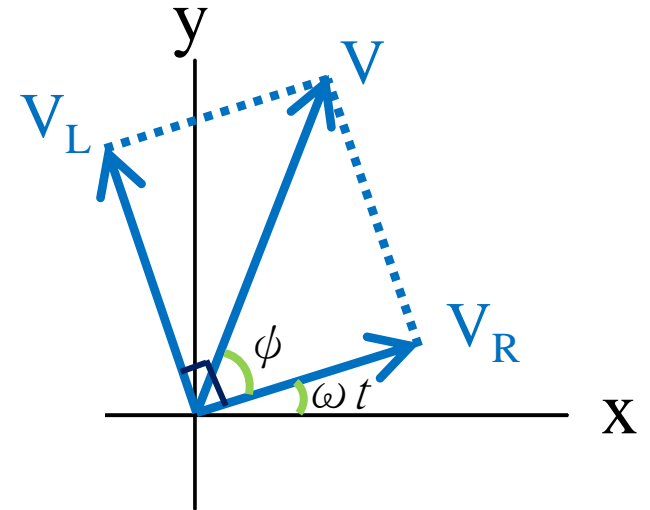
$$= LI_0 \omega \cos \left( \omega t + \frac{\pi}{2} \right)$$



$$V = V_0 \cos(\omega t + \phi)$$

$$\text{where } \begin{cases} V_0 = \sqrt{V_{R0}^2 + V_{L0}^2} = I_0 \sqrt{R^2 + (\omega L)^2} \\ \phi = \tan^{-1} \left( \frac{V_{L0}}{V_{R0}} \right) = \tan^{-1} \left( \frac{\omega L}{R} \right) \end{cases}$$

## Solution of HW12-1:


(b) RC 並聯 → 電壓  $V(t)$  一樣

$$I_R = \frac{V}{R} = \frac{V_0 \cos \omega t}{R}$$

$$I_C = \frac{dQ}{dt} = C \frac{dV}{dt}$$

$$= CV_0 \omega \cos\left(\omega t + \frac{\pi}{2}\right)$$

$$I = I_0 \cos(\omega t + \phi)$$

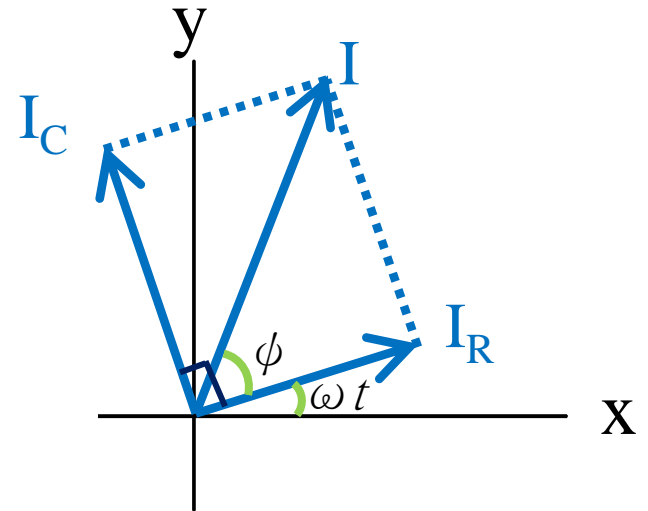


$$\text{where } \begin{cases} I_0 = \sqrt{I_{R0}^2 + I_{C0}^2} = V_0 \sqrt{\frac{1}{R^2} + (\omega C)^2} \\ \phi = \tan^{-1}\left(\frac{I_{C0}}{I_{R0}}\right) = \tan^{-1}(R\omega C) \end{cases}$$
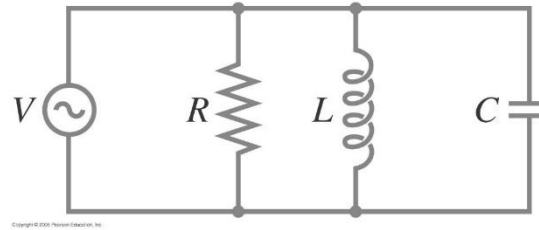
## HW11-2:

A resistor  $R$ , capacitor  $C$ , and inductor  $L$  are connected in parallel across an ac generator as shown in the Fig. 30–34. The source emf is  $V(t) = V_0 \cos(\omega t)$ .

Determine the current as a function of time (including amplitude and phase): (a) in the resistor, (b) in the inductor, (c) in the capacitor. (d) What is the total current leaving the source  $V$ ?




## Solution of HW12-2:

並聯 → 電壓  $V(t)$  一樣


$$(a) \mathbf{I}_R = \frac{V_0 \cos \omega t}{R}$$

$$(b) \mathbf{I}_C = V_0 \omega C \cos \left( \omega t + \frac{\pi}{2} \right)$$
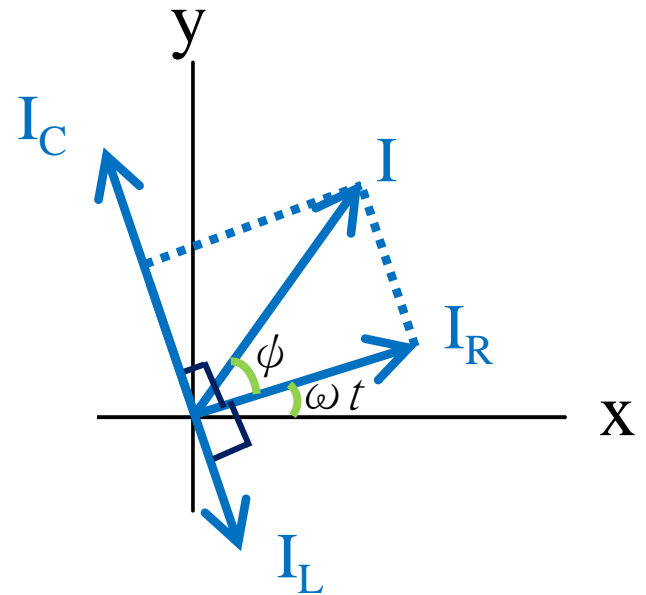
$$(c) \mathbf{I}_L = \frac{V_0}{\omega L} \cos \left( \omega t - \frac{\pi}{2} \right)$$



## Solution of HW12-2:

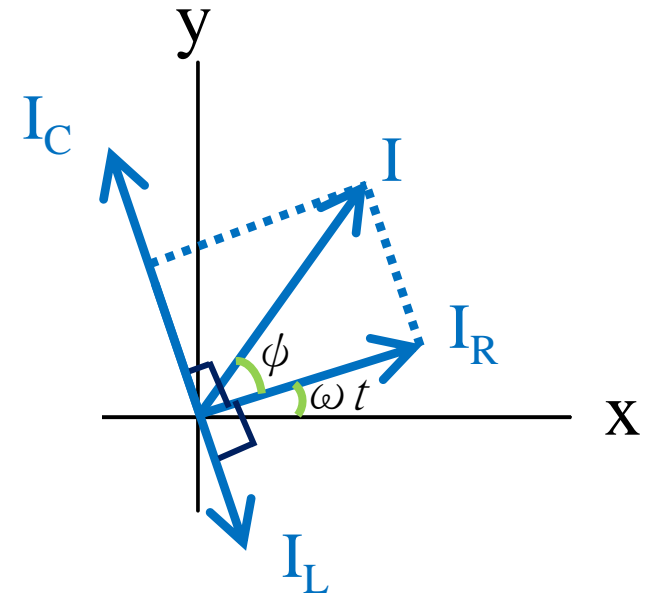


(d)  $I = I_0 \cos(\omega t + \phi)$

where  $\left\{ \begin{array}{l} I_0 = \sqrt{(I_{C0} - I_{L0})^2 + I_{R0}^2} = V_0 \sqrt{\left(\omega C - \frac{1}{\omega L}\right)^2 + \frac{1}{R^2}} \\ \phi = \tan^{-1} \left( \frac{I_{C0} - I_{L0}}{I_{R0}} \right) = \tan^{-1} \left( \frac{\omega C - \frac{1}{\omega L}}{R} \right) \end{array} \right.$


**HW11-3:** A  $N$ -turn solenoid of radius  $R$  and length  $h$  has an alternating current  $I(t) = I_0 \sin \omega t$ . Consider a point  $P$  (inside the solenoid) at radius  $r$

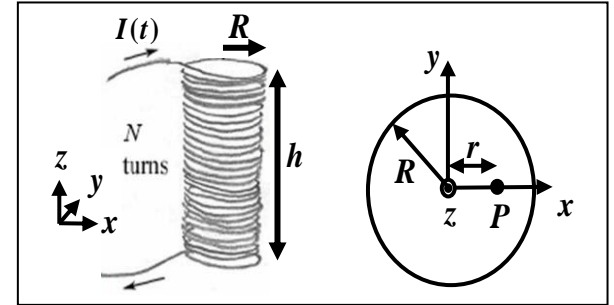- (a) Find the magnetic field  $\mathbf{B}(t)$  at  $P$  as function of time  $t$
- (b) Find the electric field  $\mathbf{E}(t)$  at  $P$ .
- (c) Find the Poynting vector  $\mathbf{S}(t)$  at  $P$




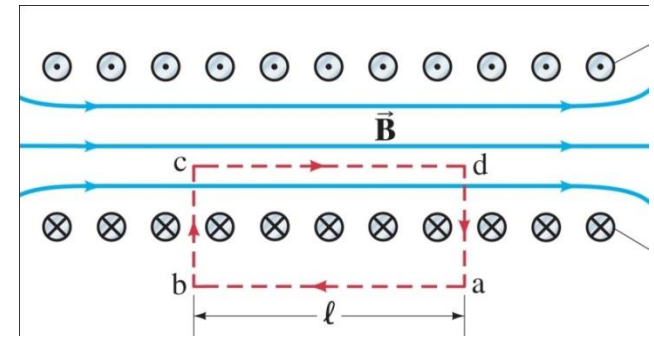
$$(a) \quad \oint \vec{B} \cdot d\vec{l} = Bl = \mu_0 I_{enc} = \mu_0 I \frac{N}{h}$$



$$\rightarrow \vec{B} = \mu_0 I_0 \frac{N}{h} \hat{z} \sin \omega t \quad (\text{or along } +z \text{ direction})$$

$$(b) \quad \oint \vec{E} \cdot d\vec{l} = -\frac{d\Phi_B}{dt} \Rightarrow E \cdot 2\pi r = -\frac{d}{dt} \iint \vec{B} \cdot d\vec{A} = -\frac{d}{dt} B \pi r^2$$

$$\Rightarrow \vec{E} = (-\hat{y}) \frac{\mu_0}{2} \frac{N}{h} r \omega I_0 \cos \omega t \quad (\text{at point } P)$$

$$(c) \quad S = \frac{1}{\mu_0} |\vec{E} \times \vec{B}| = \frac{\mu_0}{2} \left( \frac{N I_0}{h} \right)^2 r \omega \sin \omega t \cos \omega t$$

along  $-x$  at point  $P$

